

Kantronics D4-10 Analog Input Attenuator

Narrative

The Kantronics D4-10 transceiver analog input has a specification value of 50-mV P-P. Not all TNC's can be accurately adjusted down to this level and still produce a quality signal.

The unbalanced T-pad attenuator used here is designed for a 600-ohm impedance at the input and output with a target level of -30.0 dB. Thus a input level of 1.6 volts P-P (+17 dBm) results in a output level of 50-mV (-13 dBm). Using the values shown in the parts list, the attenuation is -29.722 dB with an impedance value of 597.731 ohms. The attenuator can be placed inside the DB9M shell that connects to the D4-10.

Calculations

Shown here are the formula's necessary to calculate the T-pad attenuator values with an impedance Z value of 600 ohms.

1. Determine the K value:
 $K=10^{(\text{desired dB value}/20)}$
 $K=10^{(30/20)}$
 $K=10^{(1.5)}$
 $K=31.6227$
2. Determine the value of shunt resistor R2:
 $R2=[K/(K^2-1)]*2Z$
 $R2=[31.6227/998.995]*1200$
 $R2=0.0316545*1200$
 $R2=37.985 \text{ ohms}$
3. Determine the value of series resistor R1:
 $R1=[(K-1)/(K+1)]*Z$
 $R1=[30.6227/32.6227]*600$
 $R1=0.938692996*600$
 $R1=563.215 \text{ ohms.}$

Parts List

2-each, 560-ohm 5% 1/4-watt resistor
1-each, 39-ohm 5% 1/4-watt resistor

Schematic

